

# EXTENDED

Stereo System

**Method employed in Zenith's 1960 models to control and extend the apparent separation in stereo reproduction.**

*EDITOR'S NOTE: Some of our readers may argue that the technique to be described below is an artificial method of producing an exaggerated stereo effect. Others will claim that since stereo itself is an illusion, then any method employed to enhance the illusion is justified. In any case, the system is claimed to be particularly effective when left and right speaker systems are contained in the same enclosure. We feel sure that our readers will be interested in the circuit and method used.*

**T**HE following circuit is used in Zenith's new stereo models in order to enhance the stereo effect. According to the manufacturer, the system eliminates the need for the usual small area center listening position and permits the user to control the degree of apparent separation produced. The method is said to be particularly useful in cases where all the speakers are contained in a single enclosure. As will be seen below, a sum and difference technique is used. By controlling the amount of the difference channel various degrees of the stereo effect can be produced.

The block diagram in Fig. 1 shows the basic principle of operation. The stereo cartridge supplies separate left (L) and right (R) channel signals. These signals are then applied through an automatic balance control circuit to a mixer preamplifier. Out of the mixer two types of information are obtained. These are the sum signal (L + R), which is applied to the sum amplifier, and the difference signal (L - R), which is applied to the difference amplifier. A stereo control in the difference channel determines the degree of stereo effect produced. Outputs from both amplifiers are applied to a transformer matrixing circuit. Here the information is separated and applied to the two sets of speakers used.

### Mixer Preamp Circuit

The controlling circuit governing the degree of stereo is the mixer preamp shown in Fig. 2. For the sake of convenience assume that the signals coming from the stereo cartridge are -L and -R. These signals are applied to

the wiper arms of two 3-meg. potentiometers that are ganged together. These pots are in the grid circuits of the 12AZ7 twin-triode. The controls are so wired that when the signal is increased at one grid, it is decreased at the other grid, and *vice versa*. In this manner, satisfactory balance can be obtained. The twin-triode acts as a preamp as well as a mixer so that we can obtain the sum and difference information.

With a -L signal supplied by the cartridge, there will be +L at the plate of the left preamp because of phase reversal of the tube. If we assume that the left preamp has a gain of 2, then there will be +2L at the plate. This 2L signal is applied through the 68,000-ohm resistor and the .1- $\mu$ f. capacitor to the output. Also at the plate of the left preamp is a voltage divider consisting of a 15,000-ohm resistor and a 6800-ohm resistor. At the junction of these two resistors there will be some +L signal.

*(Continued on page 156)*

Fig. 1. Block diagram of arrangement used for "extended stereo."


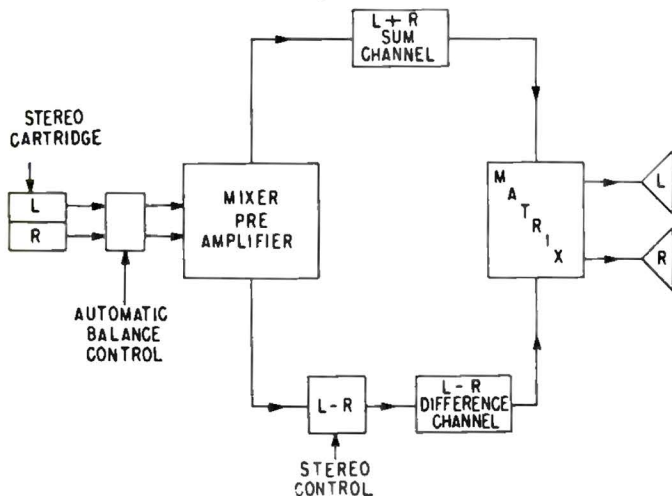


Fig. 2. The mixer-preamplifier circuit employed in Zenith sets.

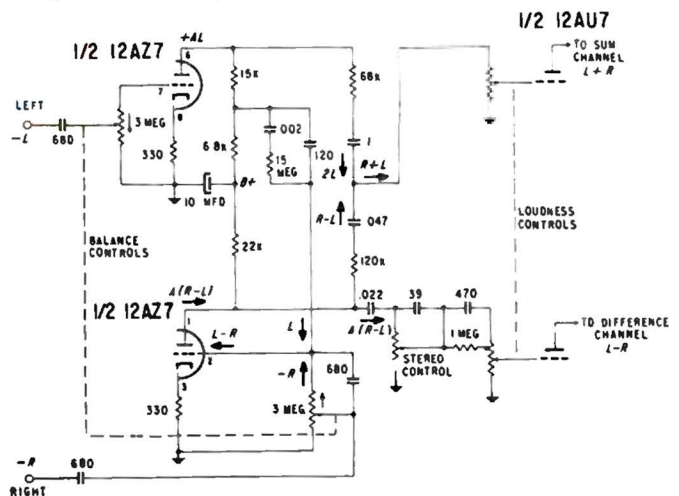

# FREE CAREER BOOKLET



to guide you to a successful future in

## ELECTRONICS RADIO-TV COMPUTERS ELECTRICAL ENGINEERING

This interesting pictorial booklet tells you how you can prepare for a dynamic career as an Electrical Engineer or Engineering Technician in many exciting, growing fields:

**MISSILES • RADAR • RESEARCH  
ELECTRICAL POWER • ROCKETRY  
AUTOMATION • AVIONICS  
SALES • DEVELOPMENT**

Get all the facts about job opportunities, length of study, courses offered, degrees you can earn, scholarships, part-time work — as well as pictures of the Milwaukee School of Engineering's educational and recreational facilities. No obligation — it's yours free.

### MILWAUKEE SCHOOL OF ENGINEERING

#### MAIL COUPON TODAY!

**MILWAUKEE SCHOOL OF ENGINEERING**  
Dept. EW-160, 1025 N. Milwaukee St.  
Milwaukee, Wisconsin MS-113

Please send FREE "Your Career" booklet  
I'm interested in  Electronics  Radio-TV  
 Computers  Electrical Engineering  
 Mechanical Engineering  
(PLEASE PRINT)

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

I'm eligible for veterans education benefits.

Discharge date \_\_\_\_\_

### Extended Stereo System

(Continued from page 50)

At the same time, -R information is being supplied to the element of the balance control that feeds the other section of the 12AZ7. Also being applied to this same element of the balance control is the L signal from the other section of the 12AZ7. Hence a composite signal, L-R, is impressed on the grid of the lower section of the mixer stage. This signal is also phase inverted by the tube so that it now becomes an (R-L) signal.

The (R-L) information is channelled into two paths. Part of this information is fed through the .022- $\mu$ f. capacitor to the stereo control, which is basically a gain control for the (R-L) difference channel. Also part of the information is fed through the 120,000-ohm resistor and the .047- $\mu$ f. capacitor and mixes with the 2L signal from the left preamp. At this point the (R-L) signal combines with the 2L signal to

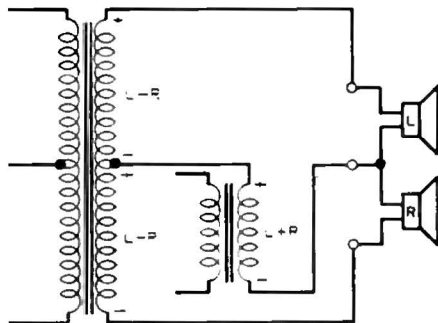


Fig. 3. Basic matrixing circuit used.

produce an (R+L) sum signal that is fed to the sum amplifier.

#### Stereo Control & Matrixing

For monophonic operation, the stereo control is at its minimum setting. Under this condition no difference signal is applied to the difference channel. All information that passes through the system is (L+R) which is subsequently channelled to both speaker systems.

For standard stereo operation, the stereo control is advanced until the sum amplifier and difference amplifier receive equal amplitude signals. Under these conditions, (L+R) and (L-R) information is supplied to the matrix and only the L information is applied to the left speaker and only the R information is applied to the right speaker. This is normal stereo operation.

For "extended stereo" operation, the stereo control is advanced further so that the (L-R) or difference-channel signal is greater than the signal applied to the sum (L+R) channel. This difference in relative level is maintained at different loudness settings since the loudness control for both sum and difference amplifiers are ganged and the gains of both channels are controlled simultaneously.

Output matrixing, or mixing of the

## PRE-PUBLICATION SPECIAL OFFER!

YOU MAY HAVE EITHER OR BOTH OF THESE BIG, HARD-COVER ELECTRONICS GUIDEBOOKS ON A

### 7-DAY FREE EXAMINATION



**COMPUTERS AND HOW THEY WORK**  
\$4.95

Here is a fact-filled, exciting guidebook to the wonder-world of electronic computers, with more than 120 illustrations and easy-to-follow tables in 10 big chapters. Step by step, you'll see and understand the workings of every type of computer ever used. This important new book illustrates the basic principles of computers with crystal-clear clarity. It's must reading for career-minded students and for electronics professionals who want a more complete knowledge of computers.

**THE ELECTRONIC EXPERIMENTER'S MANUAL**  
\$4.95



THE ELECTRONIC EXPERIMENTER'S MANUAL is a big, informative volume, containing hundreds of specially prepared diagrams and construction drawings. There are 10 individual sections, each covering a specific phase of electronic construction. One giant chapter shows projects, test equipment and special tools you can build, plus plans for a complete workshop! With just a few dollars worth of tools, and this book to guide you, you'll have the know-how you need to get started, or advance, in electronic experimentation.

**GET ONE OR BOTH FOR 7-DAY FREE EXAMINATION! MAIL THIS COUPON TODAY**

**ELECTRONICS BOOK SERVICE**  
A Division of the Ziff-Davis Publ. Co.  
One Park Avenue • New York 16, N. Y.

Gentlemen: Send me a copy of  
 COMPUTERS AND HOW THEY WORK  
 THE ELECTRONIC EXPERIMENTER'S MANUAL  
and bill me at only \$4.95 a copy plus post age. I understand that I may return the book(s) within 7 days and owe nothing \$\_\_\_\_\_ enclosed. (SAVE MONEY! Enclose payment now and we'll pay the postage.)

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

(N.Y.C. orders add 3% sale tax. EW160)



sum and difference signals in order to get the desired outputs for the speakers, is accomplished by the output transformers (Fig. 3). The secondary winding of the difference-channel (L-R) transformer is center-tapped. To this center-tapped secondary is connected the untapped secondary winding of the sum-channel (L+R) transformer. We now have two windings that are connected in series-aiding (the sum winding and the top half of the difference winding) or in series-opposing (the sum winding and the bottom half of the difference winding). There are three possible conditions of operation as follows:

1. For monophonic operation, there is no difference signal so that both speakers will receive the sum signal.

2. For standard or normal stereo operation, the output of the difference channel is equal to the output of the sum channel. Under these conditions the upper speaker has applied to it (L+R) + (L-R), or 2L. Note that this is the left information only. The lower speaker has applied to it (L+R) - (L-R), or 2R. This is the right information only.

3. For "extended stereo" operation, the output of the difference channel is greater than the sum channel. Assuming there is twice the signal in the difference channel, or 2(L-R), the signal applied to the upper speaker is (L+R) + 2(L-R), or 3L-R. The signal applied to the lower speaker is (L+R) - 2(L-R), or 3R-L. Notice that the left speaker system receives an out-of-phase component of right information along with the left information, and the right speaker system receives an out-of-phase component of left information along with the right information. The magnitude of the out-of-phase components is what determines the apparent spread of the "extended stereo" system.

NEW FOR 1960! INTRODUCTORY OFFER


# FREE! CHOOSE ANY 2 PAKETTES

WITH EVERY 12 PAKETTE ORDER

6 PAKETTE ORDERS—CHOOSE ANY 1 PAKETTE FREE

Pick your FREE PAKETTES from this listing!

- |  |   |  |   |
|--|---|--|---|
| <p><b>30 "SEALED" CIRCUITS</b><br/>Built-in resistor coupling networks. Reg. \$20. <b>\$1</b></p> <p><b>40 MOLDED CONDENSERS</b><br/>0.0001 to 1 to 1000 VDC. Oils, porcelain, black beauties. Reg. \$1. <b>\$1</b></p> <p><b>65 RESISTOR SPECIAL</b><br/>W.W. &amp; carbon, precision, power, variable, min. types, too. 1/2W to 20W. Reg. \$17. <b>\$1</b></p> <p><b>40 POWER RESISTORS</b><br/>5 to 500W to 10,000 ohms. Reg. \$15. <b>\$1</b></p> <p><b>50 TRANSISTOR COND.</b><br/>Mini condenser types. 0.00025 to 0.1 mf. In form of trans. sets. Reg. \$7. <b>\$1</b></p> <p><b>100 HALF WATTERS</b><br/>Resistor, carbon, 10 ohms to 2 meg. 100 types. Popular makes. Reg. \$10. <b>\$1</b></p> <p><b>15 "GRAIN-O-WHEAT"</b><br/>Lamps by 0.4, 1.5, 4V. For mini work. Worth 25¢ ea. <b>\$1</b></p> <p><b>70 MICA CONDENSERS</b><br/>0.00025 to 0.1 to 1000VDC. "Silver" type. 20 values. Reg. \$14. <b>\$1</b></p> <p><b>35 TON WATTERS</b><br/>10 radio &amp; TV values; 100 ohms to 500K. 57 types. Reg. \$8. <b>\$1</b></p> <p><b>15 ROTARY SWITCHES</b><br/>1, 2, 3 gang long shafts. Popular types. Reg. \$15. <b>\$1</b></p> <p><b>15 VOLUME CONTROLS</b><br/>Up to 1 meg. Singles, duals. Reg. \$20. <b>\$1</b></p> <p><b>2 SOLAR BATTERIES</b><br/>Generate power from Sun &amp; "bulb" light. 20 types of projects. Reg. \$4. <b>\$1</b></p> <p><b>20 TWIST DRILLS</b><br/>1/16 thru 1/4 with elaborated case. For electric drills. Reg. \$2.50. <b>\$1</b></p> <p><b>24 ARTISTS BRUSHES</b><br/>1 to 1 1/2 sizes. 100% pure camel hair. <b>\$1</b></p> | <p><b>40 HI Q CONDENSERS</b><br/>NP0's, standard types to 20 values. Finest price. Quality. Reg. \$9. <b>\$1</b></p> <p><b>60 TERMINAL STRIPS</b><br/>Solder lug type, 0.1 to 10 lugs. Used in circuit design. Reg. \$1. <b>\$1</b></p> <p><b>\$25 SURPRISE PAKETTE</b><br/>Wide variety of radio parts. Reg. \$25. <b>\$1</b></p> <p><b>70 TUBULAR CONDENSERS</b><br/>20 values, 0.1 to 100 VDC. Reg. \$10. <b>\$1</b></p> <p><b>30 "SILVER" MICAS</b><br/>1 to 50 values. Finest made. Reg. \$15. <b>\$1</b></p> <p><b>70 INSULATED RESIST'S</b><br/>Carbon, 1 &amp; 5/2 watt. 10 ohms to 10 meg. 30 values. 1/2, 1, 2W. Reg. \$15. <b>\$1</b></p> <p><b>10 RCA PLUG 'N JACK SETS</b><br/>Matched pairs, for tuners, amps, too. <b>\$1</b></p> <p><b>300-FT. HOOK-UP WIRE</b><br/>10 thru 24. Plastic, 1/4 class, insulated. Assorted. Nifty lead ends. <b>\$1</b></p> <p><b>60 RADIO-TV KNOBS</b><br/>Assorted, set screw type. 100. Plastic. 2 to 4 dia. Some \$1 ea. <b>\$1</b></p> <p><b>50 ONE PERCENT-ERS</b><br/>Precision carbon film resistors. 15 values. 100 ohms to 1 meg. Reg. \$20. <b>\$1</b></p> <p><b>60 CONDENSER SPECIAL</b><br/>Oil, mica, electrolytic, mica, disc. Reg. \$15. <b>\$1</b></p> <p><b>5 ROLLS MICRO-WIRE</b><br/>24, 4, 3/32, Assorted colors, insulation. Tinned. Reg. \$5. <b>\$1</b></p> <p><b>1500 PCS. HARDWARE</b><br/>Nuts, bolts, screws, brackets, etc. Handy shop packets. <b>\$1</b></p> <p><b>3 HOBBY TRANSISTORS</b><br/>For experimental &amp; shop use. Specs. like known. Worth \$1 ea. <b>\$1</b></p> <p><b>WORLD'S SMALLEST RADIO</b><br/>Kit. Minimum power. Great. Lasts for life. Tree, all parts, instructions. <b>\$1</b></p> <p><b>12 GERMANIUM DIODES</b><br/>For radio &amp; TV detectors, limiters, rectifiers. Glass, sealed, long leads. <b>\$1</b></p> <p><b>125 RESISTORS</b><br/>Non-insulated, 10 popular values; 1/2, 1, 2W, 1/2 to 10 ohms to 10 meg. Reg. \$15. <b>\$1</b></p> | <p><b>10-IN-1 PAKETTE</b><br/>Incl. diodes, resistors, electros, sockets, lites, wire, knobs, controls. <b>\$1</b></p> <p><b>TRANSISTOR RADIO BASIC</b><br/>Incl. transistor &amp; socket, diode, loopstick. In handy pak. <b>\$1</b></p> <p><b>2 POWER TRANSISTORS</b><br/>Handles 10 watts. For audio circuits in cars, etc. Worth \$10 ea. <b>\$1</b></p> <p><b>2 SILICON RECTIFIERS</b><br/>500 mil. Actual leads. Size of 1W resistors. Reg. \$3 ea. <b>\$1</b></p> <p><b>8-PC. NUTDRIVER SET</b><br/>Molded, lucite handle. Steel socket wrenches. 1/16, 7/32, 1/4, 5/16, 11/32, 7/16". In car. <b>\$1</b></p> <p><b>10 PANEL SWITCHES</b><br/>115 VAC micro, slide, etc. Some worth \$1. <b>\$1</b></p> <p><b>4 OUTPUT XFMR'S</b><br/>500, 400, 300, etc. Open frame types. Some worth \$2.50 ea. <b>\$1</b></p> <p><b>2 FLEA POWER MOTORS</b><br/>1/2 W. VAC. Powerful. 100's of controls. <b>\$1</b></p> <p><b>40 TUBE SOCKETS</b><br/>4, 5, 15, 7, 8, 9 pins. Details, min. types. Some shield, mica, ceramic. Reg. \$10. <b>\$1</b></p> <p><b>30 PILOT LITES</b><br/>Mini lites &amp; screw types. 1/2 to 1/4 W. <b>\$1</b></p> <p><b>40 DISC CONDENSERS</b><br/>Incl. world's finest; only 1" x 1/2" dia. <b>\$1</b></p> | <p><b>15 "POLY PAKETTES"</b><br/>Incl. poly boxes, valv. ast. sizes. For radio, TV submini parts. <b>\$1</b></p> <p><b>15 ELECTROLYTICS</b><br/>PF &amp; tubular paper &amp; cap types. Single, duals &amp; triple values. 10 to 500 µf to 450 VDC. Reg. \$20. <b>\$1</b></p> <p><b>100 CERAMIC SPECIAL</b><br/>Incl. NP0's, NP0's, moldeds, tubular, dog bones. 25 values. <b>\$1</b></p> <p><b>75 ONE WATTERS</b><br/>Resistors, incl. 1 &amp; 5/2 watt. 20 to 100 values. Reg. \$18. <b>\$1</b></p> <p><b>2 POSTAGE STAMP MIKES</b><br/>Crystal. By Brush. 1/2 sq. in. Nifty, hide-away unit. 100 to 7000 cps response. <b>\$1</b></p> <p><b>7 SILICON DIODES</b><br/>Used in government &amp; "space" work. 1N21, 1N22, etc. Worth \$10 ea. <b>\$1</b></p> <p><b>70 COILS &amp; CHOKES</b><br/>RF, ant. osc. slug-tuned, &amp; IF styles. 15 types. Reg. \$22. <b>\$1</b></p> <p><b>60 PLUGS &amp; REC'T'S</b><br/>Power, battery, audio. 15 types. <b>\$1</b></p> <p><b>15 POLY VIALS</b><br/>For stacking submini &amp; transistor parts. EZ to see, to read, to "stack". Ass. sizes. <b>\$1</b></p> <p><b>CRYSTAL PHONE</b><br/>Use as mike tool. W/ card &amp; plug set. Hearing aid type. 100 to 9000 cps resp. <b>\$1</b></p> |
|--|---|--|---|

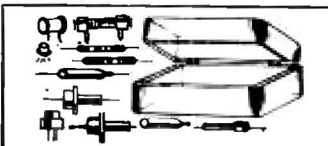

**WHAT IS LEKTRON'S PAKETTE?**  
It is Lektron's newest method of packaging radio-TV parts assortments in clear, lucite boxes. Each Pakette box features a "snap-top" cover and is easily stackable to fit any shelf or bench, yet your components are always clearly visible. This box alone is worth up to \$1.00. You save up to \$50 to \$55 on parts, too—and get bigger quantities than ever before.

MINIMUM \$2.00 ORDERS! USE AS ORD.-GRAM

## CHRISTMAS TVI

By J. T. SWANSON

THE OFTEN strange nature of interference was dramatized again last Christmas. The second set of the house, working on its built-in antenna in the living room, began to show intermittent vertical sync and horizontal flashes a few days before the holiday. Just about any movement in the room would bring on the symptoms. Moving the set to another room eliminated the trouble. Decorations on the Christmas tree were prime suspects, but the symptoms persisted when the bulbs were unplugged.

The tree was also decorated with such metallic material as tinsel and "icicles." Shaking a bunch of "icicles" brought the symptoms in severe form. Experimentally, one icicle was held in each hand and they were moved about to make intermittent contact. This induced the flashes and vertical slipping! Evidently these strips, with their invisible oxide coatings, acted as semiconductors when they made intermittent contact. They were probably detecting some strong, local signals and yielding a cross-modulation product that interfered with sync pulses.

## FREE! GIANT BARGAIN CATALOG

Due to the larger physical size of a few assortments, poly packs are used.

Include check or M.O. with sufficient postage: excess returned. C.O.D. orders, 25% down; rated, net 30 days. INCLUDE POSTAL ZONE in address. (Canada postage, 48¢ 1st lb.; 28¢ ea. additional lb.)

My FREE PAKETTES are:

1. \_\_\_\_\_
  2. \_\_\_\_\_
- Check each item wanted
  - Return ad with order
  - Avg. wt. 1 lb. per Pakette
  - Each Pakette guaranteed

## BEST IN HI-FI VALUES!

NO DELAY SERVICE

All orders rushed to you in factory-sealed cartons.

Write for free catalog.

audion 25-W Oxford Road  
Massapequa, New York



## LOOK

NO FURTHER... IF YOU'RE UNHAPPY WITH "HI" HI-FI PRICES. WRITE FOR OUR UNUSUAL AUDIO CATALOG. KEY ELECTRONICS CO. 120-C Liberty St., N. Y. 6. Phone CLOverdale 8-4288

## engineering degree in 27 mos.

Become an Electronics Engineer. Share rewards awaiting college men... higher income, rapid advancement. Important firms visit Tri-State to interview seniors. Bachelor of Science Degree in 27 months in Electrical (Electronics or Power major), Mechanical, Civil, Aeronautical, Chemical Engineering. In 36 months a B.S. in Business Administration (General Business, Accounting, Motor Transport Management majors). For earnest, capable students. Small classes. More professional class hours. Well-equipped labs. Dorms. Campus. Modest costs. Year-round operation. Enter Mar., June, Sept., Jan. Founded 1884. Write J. H. McCarthy, Director of Admissions, for Catalog and "Your Career" Book.

**LEKTRON** 133 Everett Ave. Chelsea 50, Mass.

**TRI-STATE COLLEGE**  
1610 College Ave., Angola, Indiana